

# **ECE 65: Components & Circuits Lab**

## **Lecture 9**

### **Diode waveform shaping circuits**

### **Clamp circuits**


Reference notes: sections 2.9

Sedra & Smith (7<sup>th</sup> Ed): sections 4.4-4.6

Saharnaz Baghdadchi

# Course map



## 2. Diodes

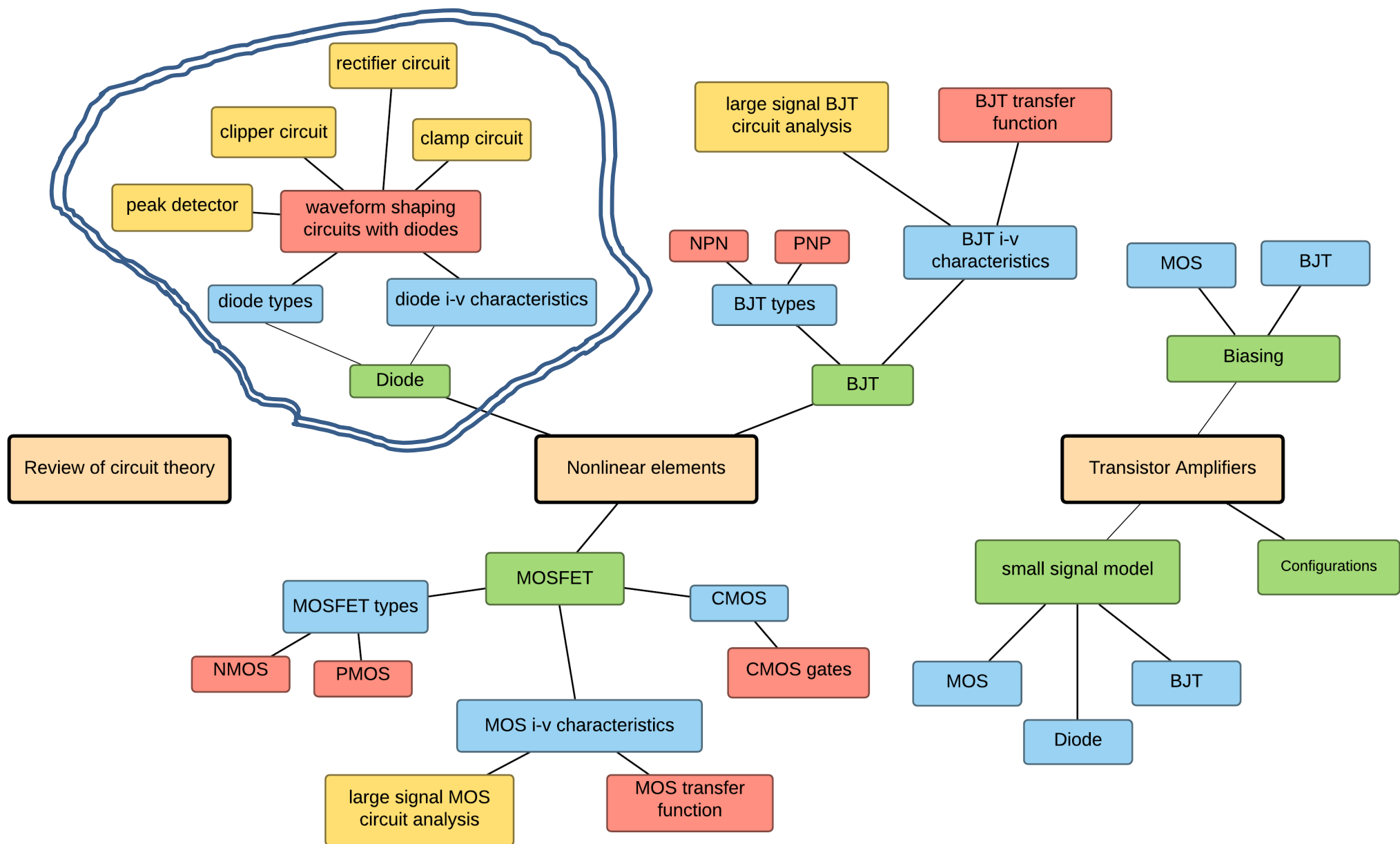

# Clamp circuit and peak detector circuit



Ideal peak detector:

$$v_o = V_p - V_{D0}$$

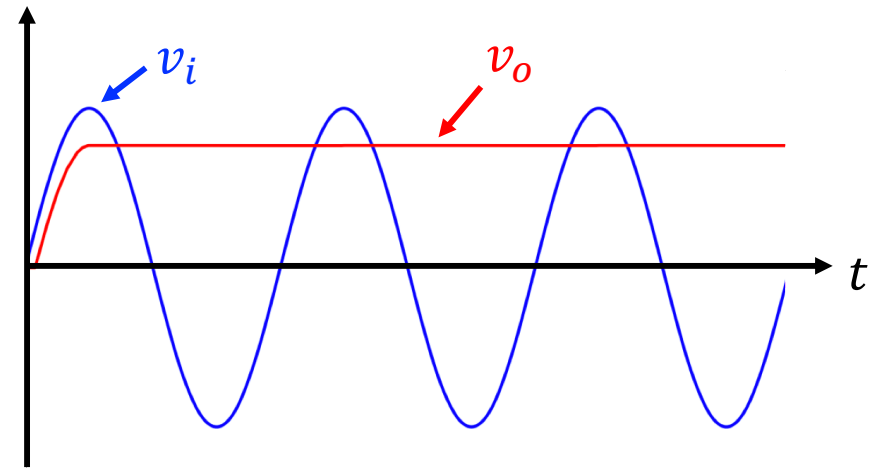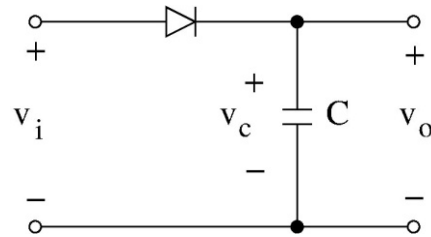


Clamp circuit:

$$v_o = v_i - (V_p - V_{D0})$$

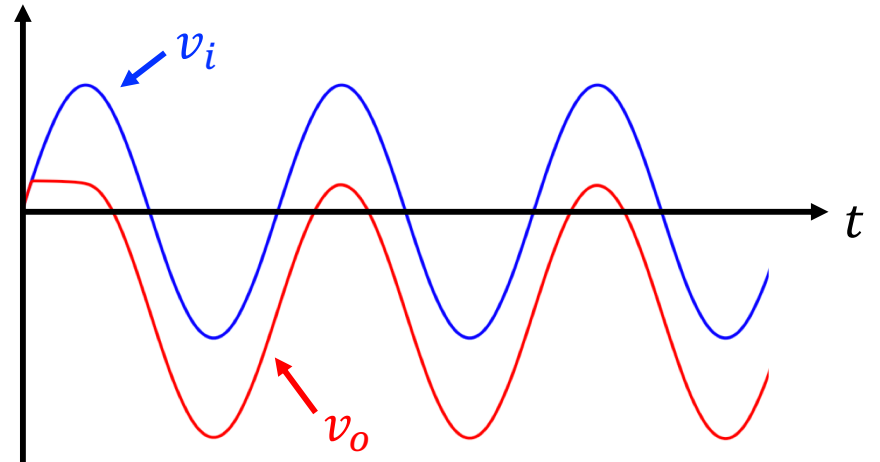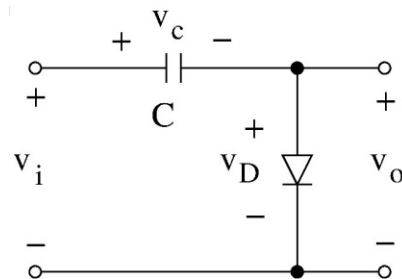


# Clamp Circuit

$$v_D = -v_c + v_i$$

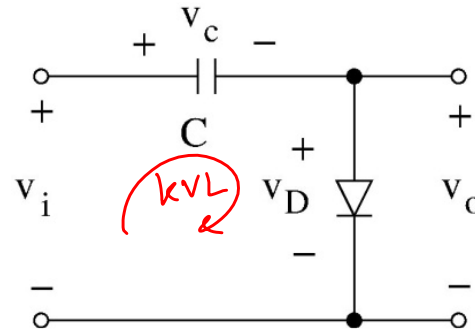

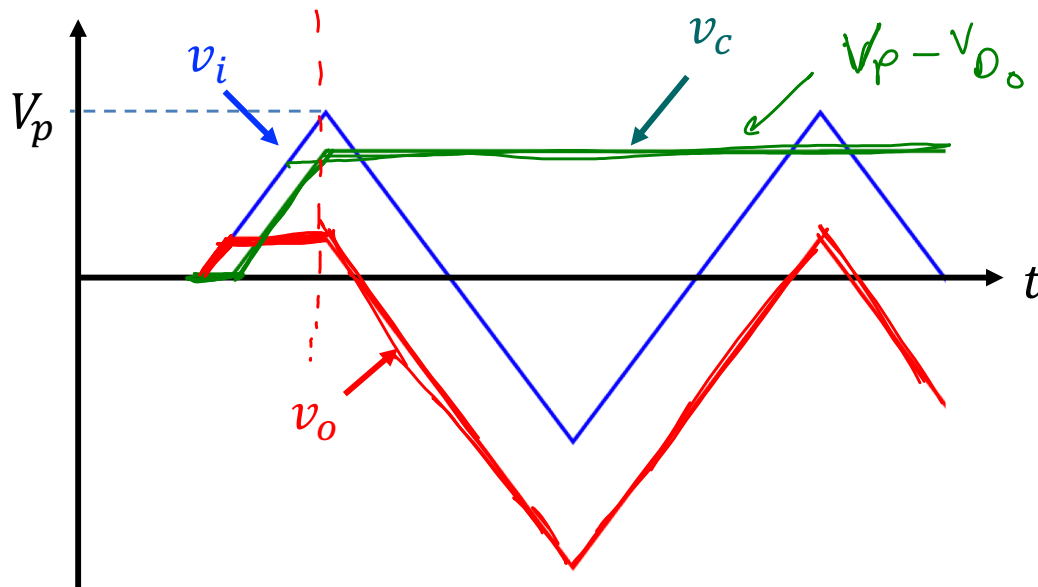The diode turns OFF when the capacitor is charged to  $v_c = \underline{V_p - V_{D0}}$





$$\underline{v_o = v_D = v_i - v_c}$$


Diode off:

$$v_o = \underline{v_i} - (V_p - V_{D0})$$

# Clamp Circuit with a Load

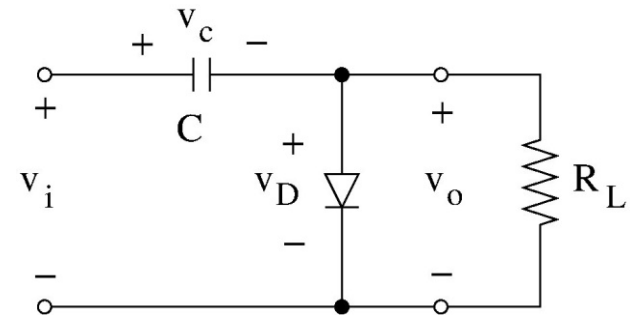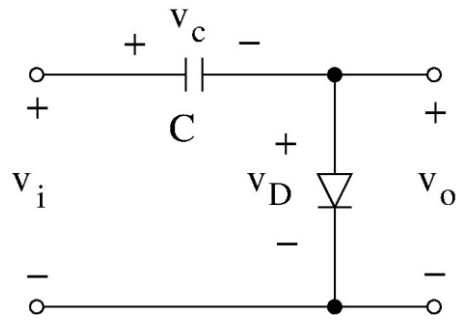


$$\tau = CR_L$$

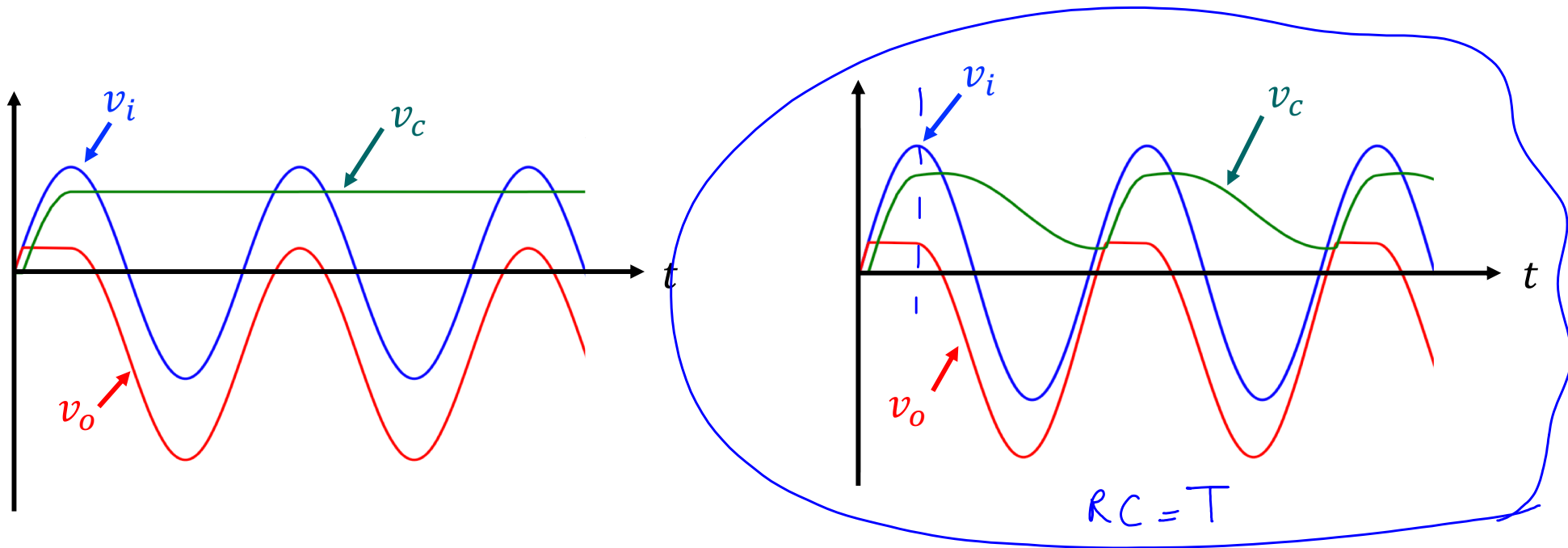

If  $\tau = R_L C \gg T$  capacitor does not discharge substantially and clamp circuits work fine

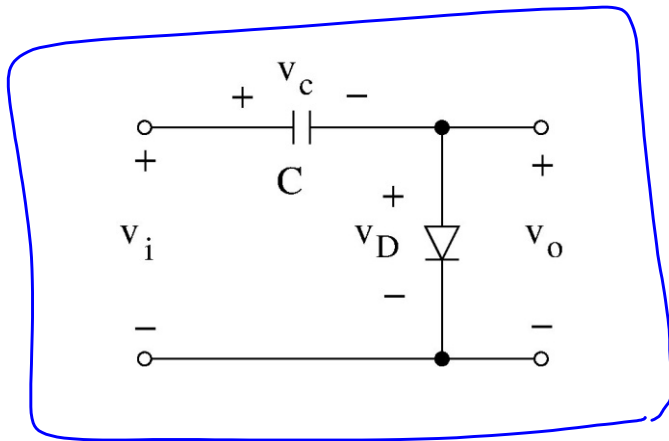
# Voltage shift in a clamp circuit can be adjusted



$$V_c = V_p - V_{D_0}$$

$$V_o = -V_c + V_i$$


$$V_o = V_i - (V_p - V_{D_0})$$

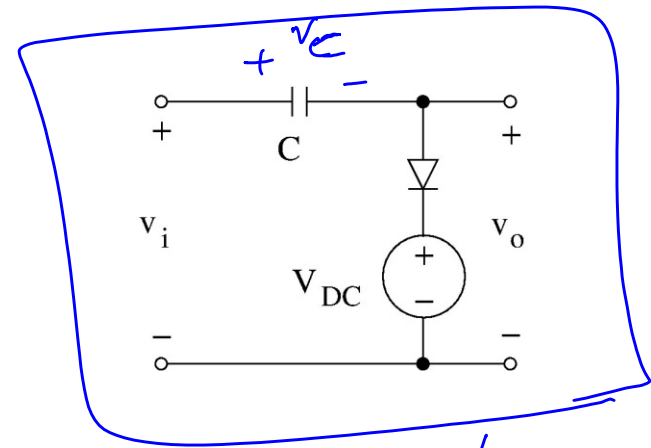

$$V_c = V_p - (V_{D_0} + V_{DC})$$

$$V_o = -V_c + V_i$$

$$= V_i - (V_p - V_{D_0} - V_{DC})$$


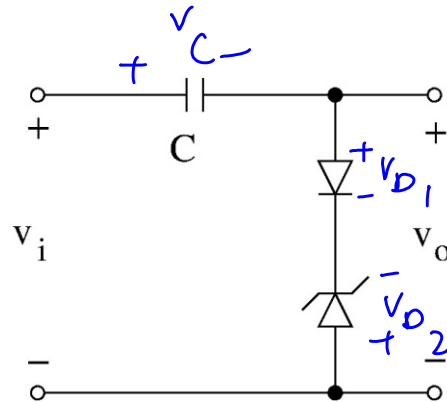


$$V_o = -V_c + V_i$$

$$= V_i - (V_p - V_{D_0} - V_Z)$$

# Clamp circuit can introduce a “positive” shift by reversing the diode terminals

Peak detector (diode is reversed):

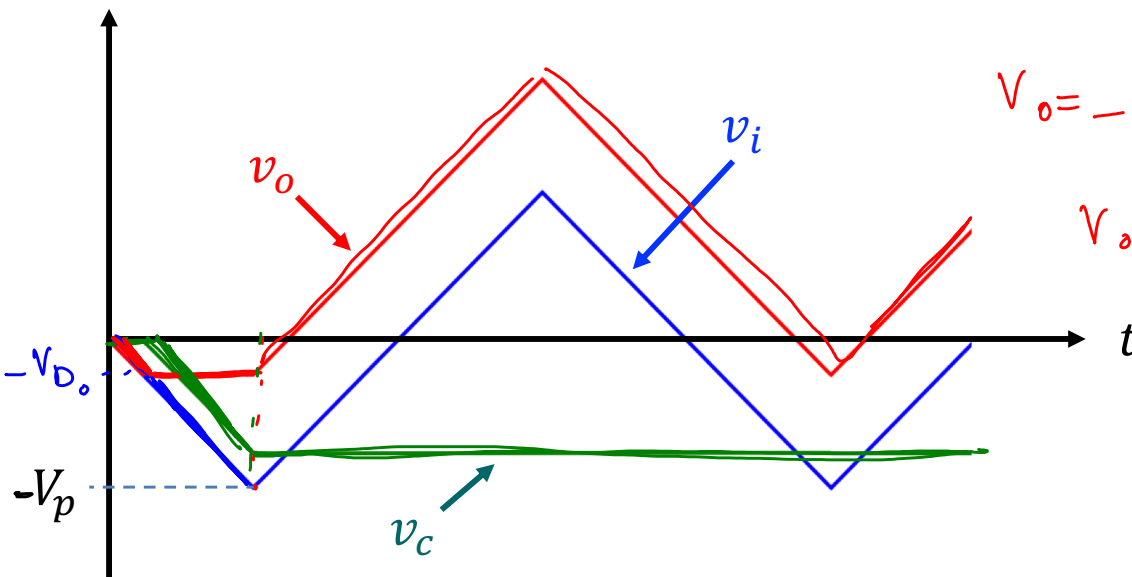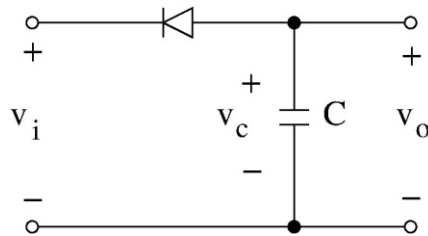


$$V_o = -V_c + V_i$$

$$V_o = -(-V_p + V_{D0}) + V_i$$

$$V_o = V_i + (V_p - V_{D0})$$

After the diode turned off

Clamp circuit (diode reversed):

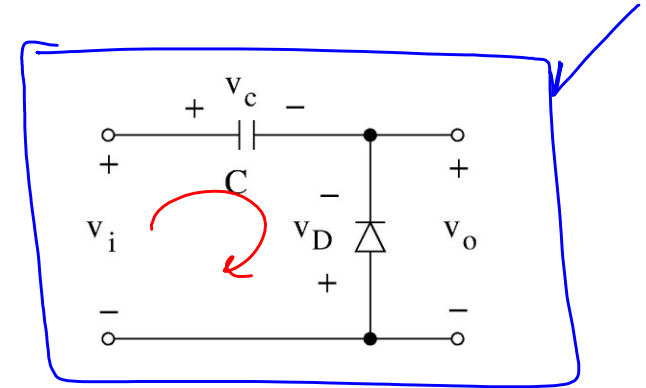

$$V_D = -V_i + V_c = -V_i$$

$$V_o = -V_D$$


$$\Rightarrow V_o = +V_i$$

$$V_o = -V_{D0}$$

$$V_c = V_i + V_{D0}$$


$$V_c = -V_p + V_{D0}$$
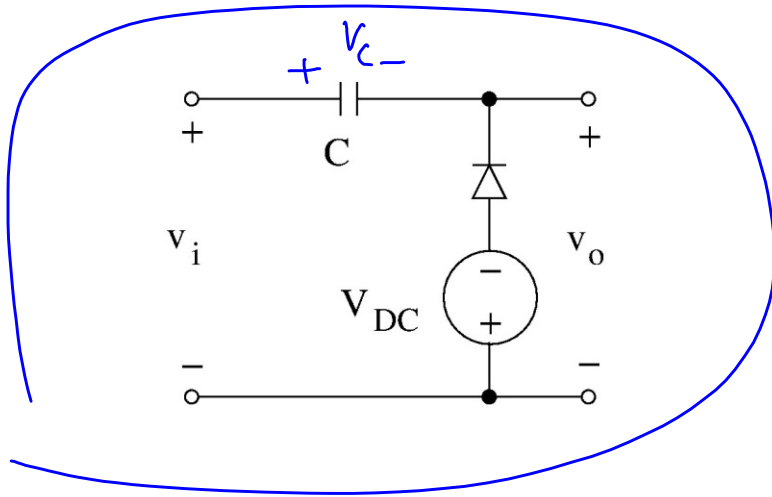
# The positive shift can also be adjusted.



$$V_c = -V_p + V_{DC} + V_{D_o}$$

$$V_o = V_i + (V_p - V_{DC} - V_{D_o})$$

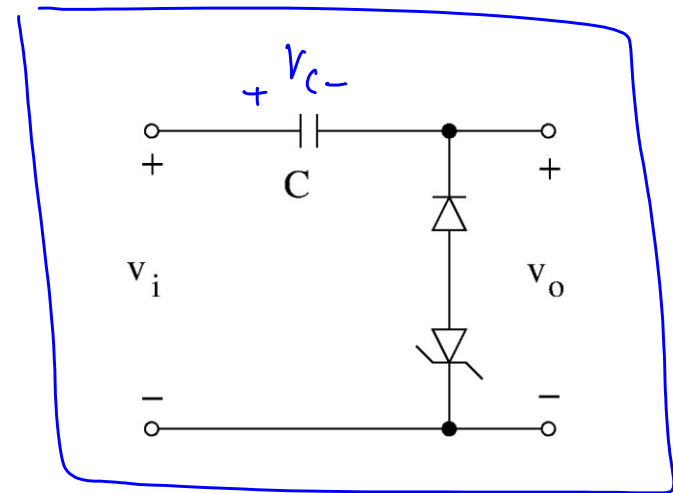


$$V_o = V_i + (V_p - V_z - V_{D_o})$$


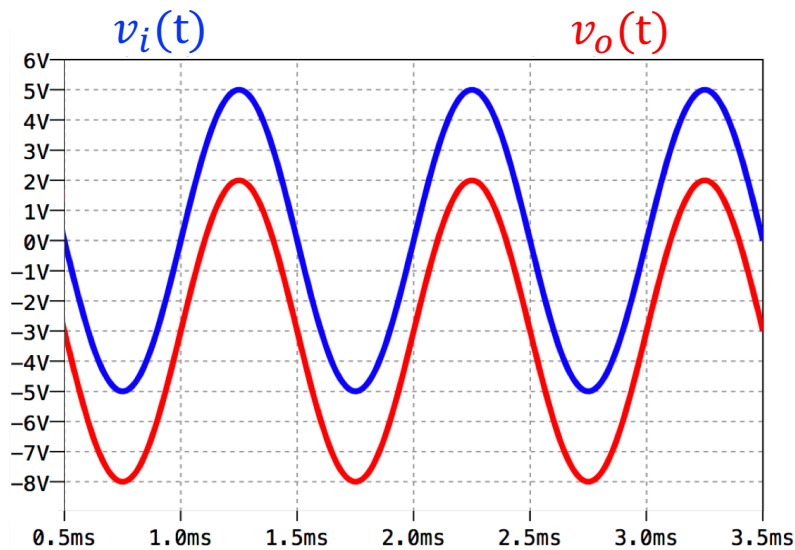
## Lecture 9 reading quiz

Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?



# Discussion question 1

Consider a sinusoidal source  $v_i(t) = 10 \sin(\omega t) \text{ V}$ . Using a DC power supply, design a clamp circuit that adds a DC offset of 5V to  $v_i(t)$ . Draw two cycles of the input and output voltage waveforms.

# Discussion question 1

Consider a sinusoidal source  $v_i(t) = 10 \sin(\omega t) \text{ V}$ . Using a DC power supply, design a clamp circuit that adds a DC offset of 5V to  $v_i(t)$ . Draw two cycles of the input and output voltage waveforms.

- Check the lecture notes to see the structure of the clamp circuit that can add a positive DC shift to input signals.
  - You can use the equations included in the lecture notes to find the required amplitude of VDC to have the +5V DC shift.
  - After drawing the circuit structure, solve the circuit to find  $v_{out}$  as a function of  $v_i$  for different time intervals.
  - You need to find the minimum value of  $v_i$  to turn on the diode. You also need to find out for how long the diode can stay on and what happens when the diode turns off.
  - Draw  $v_i(t)$  and  $v_{out}(t)$  on the same graph.
- 
- You can also draw the clamp circuit structure with a DC source with an unknown amplitude and solve the circuit to find the amplitude of the DC source.

# Clicker question 1.

In the circuit below,  $v_i(t) = 10 \sin(\omega t)$  where  $\omega = 1000 \text{ rad/s}$ ,  $v_o(0) = 0$ .  $V_{D0} = 0.7 \text{ V}$

What is the value of  $v_o(t)$  at  $t = 2 \text{ ms}$ ?

A.  $v_o(t = 2 \text{ ms}) = 1.8 \text{ V}$

B.  $v_o(t = 2 \text{ ms}) = 6.4 \text{ V}$

C.  $v_o(t = 2 \text{ ms}) = 2.7 \text{ V}$

